



ARRL Periodicals Archive – Search Results

A membership benefit of ARRL and the ARRL Technical Information Service

ARRL Members: You may print a copy for personal use. Any other use of the information requires permission (see Copyright/Reprint Notice below).

Need a higher quality reprint or scan? Some of the scans contained within the periodical archive were produced with older imaging technology. If you require a higher quality reprint or scan, please contact the ARRL Technical Information Service for assistance. Photocopies are \$3 for ARRL members, \$5 for nonmembers. For members, TIS can send the photocopies immediately and include an invoice. Nonmembers must prepay. Details are available at www.arrl.org/tis or email photocopy@arrl.org.

QST on CD-ROM: Annual CD-ROMs are available for recent publication years. For details and ordering information, visit www.arrl.org/qst.

Non-Members: Get access to the ARRL Periodicals Archive when you join ARRL today at www.arrl.org/join. For a complete list of membership benefits, visit www.arrl.org/benefits.

Copyright/Reprint Notice

In general, all ARRL content is copyrighted. ARRL articles, pages, or documents—printed and online—are not in the public domain. Therefore, they may not be freely distributed or copied. Additionally, no part of this document may be copied, sold to third parties, or otherwise commercially exploited without the explicit prior written consent of ARRL. You cannot post this document to a Web site or otherwise distribute it to others through any electronic medium.

For permission to quote or reprint material from ARRL, send a request including the issue date, a description of the material requested, and a description of where you intend to use the reprinted material to the ARRL Editorial & Production Department: permission@arrl.org.


QST Issue: Feb 1950

Title: Two-Band Antenna-Matching Networks - Part III

Author: John Marshall, W0ARL

[Click Here to Report a Problem with this File](#)

ADVERTISEMENT

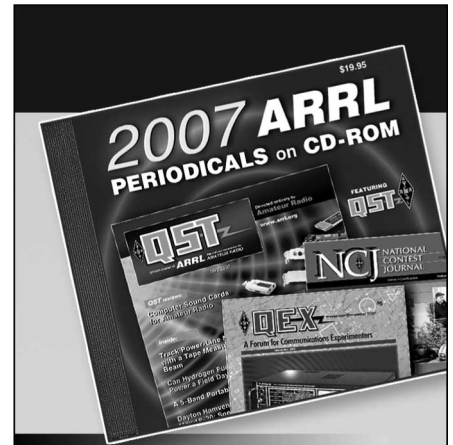

ARRL Periodicals on CD-ROM

ARRL's popular journals are available on a compact, fully-searchable CD-ROM. Every word and photo published throughout the year is included!

- **QST** The official membership journal of ARRL
- **NCJ** National Contest Journal
- **QEX** Forum for Communications Experimenters

SEARCH the full text of every article by entering titles, call signs, names—almost any word. SEE every word, photo (including color images), drawing and table in technical and general-interest features, columns and product reviews, plus all advertisements. PRINT what you see, or copy it into other applications.

System Requirements: Microsoft Windows™ and Macintosh systems, using the industry standard Adobe Acrobat Reader® (included).

ARRL Periodicals on CD-ROM \$19.95* per set.

- 2007 Edition, ARRL Order No. 1204
- 2006 Edition, ARRL Order No. 9841
- 2005 Edition, ARRL Order No. 9574
- 2004 Edition, ARRL Order No. 9396
- 2003 Edition, ARRL Order No. 9124
- 2002 Edition, ARRL Order No. 8802
- 2001 Edition, ARRL Order No. 8632
- 2000 Edition, ARRL Order No. 8209
- 1999 Edition, ARRL Order No. 7881
- 1998 Edition, ARRL Order No. 7377
- 1997 Edition, ARRL Order No. 6729
- 1996 Edition, ARRL Order No. 6109
- 1995 Edition, ARRL Order No. 5579

*plus shipping and handling



ARRL The national association for AMATEUR RADIO

SHOP DIRECT or call for a dealer near you.
ONLINE WWW.ARRL.ORG/SHOP
ORDER TOLL-FREE 888/277-5289 (US)

Two-Band Antenna-Matching Networks

Practical Application of Formulas

PART III

BY JOHN G. MARSHALL,* WØARL

[This is the third and concluding part of a series of three installments. The first and second parts of this article appeared in the October and November, 1949, issues of QST. — Ed.]

To demonstrate the use of these networks and their formulas, examples are given of a simple antenna operating on its fundamental and second-harmonic frequencies, using various types of transmission lines. Driving-point impedances (d.p.i.) of 75 and 1500 ohms are assumed for f_1 and f_2 , respectively. These may not be the exact values for individual cases, but they are typical and serve here to demonstrate the use of the formulas. The examples are worked out to normal slide-rule accuracy which should be entirely adequate, since the error in determining the d.p.i. in each case is likely to be much greater.

The relationships existing between Z_0 , Z_1 and Z_2 determine which of the networks is needed for any certain example. Table I shows the proper network and formulas to use for any combination of Z_0 , Z_1 and Z_2 likely to exist in present-day amateur antennas. These formulas are the same as those discussed earlier.

Example 1

Given: A simple center-fed antenna operating on its fundamental and second-harmonic frequencies, using a 53-ohm line. The d.p.i. is 75 ohms on f_1 and 1500 ohms on f_2 . Transmitter power is one kilowatt output.

Solution: Since f_2 is twice f_1 , $K = 2$. With $Z_0 = 53$ ohms, $Z_1 = 75$ ohms and $Z_2 = 1500$ ohms, this example falls into the general case where $Z_0 < Z_1$ and Z_2 . The table shows that the network of Fig. 5 and its associated formulas are applicable. Substituting numerical values in these formulas, we have the following:

$$X_{P1} = 75 \sqrt{\frac{53}{75 - 53}} = 116 \text{ ohms,}$$

and

$$X_{P2} = -1500 \sqrt{\frac{53}{1500 - 53}} = -287 \text{ ohms.}$$

Then,

$$X_{LP} = \frac{(116)(2^2 - 1)}{2 \left(2 - \frac{116}{287} \right)} = 72.4 \text{ ohms,}$$

and

$$X_{CP} = \frac{(-287)(2^2 - 1)}{\frac{-287}{116} - 2} = 193 \text{ ohms.}$$

Since

$$X_{B1} = -53 \sqrt{\frac{75}{53}} - 1 = -34.1 \text{ ohms,}$$

and

$$X_{B2} = 53 \sqrt{\frac{1500}{53}} - 1 = 277 \text{ ohms,}$$

$$X_{LS} = \frac{[(2)(277)] - [-34.1]}{(2)(2^2 - 1)} = 98 \text{ ohms,}$$

and

$$X_{CS} = \frac{2[277] - [(2)(-34.1)]}{(2)(2^2 - 1)} = 115 \text{ ohms.}$$

$$E_{CP} = \sqrt{(2)(1000)(1500)} = 1732 \text{ volts.}$$

$$E_{CS} = 115 \sqrt{\frac{(2)(1000)}{53}} = 706 \text{ volts.}$$

Example 2

Given: Same as Example 1, except that the line has a characteristic impedance of 75 ohms.

Solution: With f_2 twice f_1 , $K = 2$. With Z_0 and $Z_1 = 75$ ohms and $Z_2 = 1500$ ohms, this example falls into the case of $Z_0 = Z_1 < Z_2$. Table I shows that the network of Fig. 6 and its associated formulas are applicable. Substituting numerical values in these formulas, we have:

* Box 6023, Kansas City 4, Mo.

TABLE I					
GENERAL CASE	NETWORK SCHEMATIC	CIRCUIT-ELEMENT REACTANCE AT f_1		UNMODULATED PEAK CAPACITOR VOLTAGES	
		PARALLEL	SERIES	ACROSS C_p	ACROSS C_s
$Z_0 < Z_1$ and Z_2	<p style="text-align: center;">FIG. 5</p>	$X_{LP} = \frac{X_{P1}(K^2-1)}{K(K-\frac{X_{P1}}{X_{P2}})} \Omega$ $X_{CP} = \frac{X_{P2}(K^2-1)}{X_{P2}-K} \Omega$ <p style="text-align: center;">where</p> $X_{P1} = Z_1 \sqrt{\frac{Z_0}{Z_1-Z_0}}$ $X_{P2} = -Z_2 \sqrt{\frac{Z_0}{Z_2-Z_0}}$	$X_{L,S} = \frac{KX_{B2}-X_{B1}}{2(K^2-1)} \Omega$ $X_{CS} = K \frac{X_{B2}-KX_{B1}}{2(K^2-1)}$ <p style="text-align: center;">where</p> $X_{B1} = Z_0 \sqrt{\frac{Z_1}{Z_0}-1}$ $X_{B2} = Z_0 \sqrt{\frac{Z_2}{Z_0}-1}$	$E_{CP} = \sqrt{2W(d.p.i.)}$ <p style="text-align: center;">Use the larger of Z_1 and Z_2 for d.p.i.</p>	$E_{CS} = X_{CS} \sqrt{\frac{2W}{Z_0}}$
$Z_1 < Z_0 < Z_2$ $Z_0 = Z_1 < Z_2$ $Z_1 < Z_0 = Z_2$	<p style="text-align: center;">FIG. 6</p>	$X_{LP} = Z_0 \sqrt{\frac{K^2 Z_2 - \frac{Z_1}{K^2}}{K^2 Z_2 (\frac{Z_0}{Z_1}-1) + Z_1 (\frac{Z_0}{Z_2}-1)}} \Omega$ <p style="text-align: center;">and</p> $X_{CP} = K \sqrt{Z_1 Z_2 \frac{K^2 Z_2 - \frac{Z_1}{K^2}}{K^2 Z_1 (\frac{Z_0}{Z_2}-1) + Z_2 (\frac{Z_0}{Z_1}-1)}} \Omega$	$X_{L,S} = \frac{KX_{B2}-X_{B1}}{2(K^2-1)} \Omega$ $X_{CS} = K \frac{X_{B2}-KX_{B1}}{2(K^2-1)}$ <p style="text-align: center;">where</p> $X_{B1} = \frac{X_{CP}}{1+(\frac{X_{CP}}{Z_1})^2} - \frac{X_{LP}}{1+(\frac{X_{LP}}{Z_0})^2}$ $X_{B2} = \frac{KX_{CP}}{K^2+(\frac{X_{CP}}{Z_2})^2} - \frac{KX_{LP}}{1+(\frac{KX_{LP}}{Z_0})^2}$	$E_{CP} = \sqrt{2WZ_2}$	$E_{CS} = X_{CS} \sqrt{\frac{2WZ_0}{Z_0 \cos \phi}}$ <p style="text-align: center;">where</p> $\tan \phi = \frac{Z_0}{X_{LP}}$
Z_1 and $Z_2 < Z_0$	<p style="text-align: center;">FIG. 7</p>	$X_{LP} = \frac{X_{P1}(K^2-1)}{K(K-\frac{X_{P1}}{X_{P2}})} \Omega$ $X_{CP} = \frac{X_{P2}(K^2-1)}{X_{P2}-K} \Omega$ <p style="text-align: center;">where</p> $X_{P1} = Z_0 \sqrt{\frac{Z_1}{Z_0-Z_1}}$ $X_{P2} = -Z_0 \sqrt{\frac{Z_2}{Z_0-Z_2}}$	$X_{L,S} = \frac{KX_{B2}-X_{B1}}{2(K^2-1)} \Omega$ $X_{CS} = K \frac{X_{B2}-KX_{B1}}{2(K^2-1)}$ <p style="text-align: center;">where</p> $X_{B1} = -Z_1 \sqrt{\frac{Z_0}{Z_1}-1}$ $X_{B2} = Z_2 \sqrt{\frac{Z_0}{Z_2}-1}$	$E_{CP} = \sqrt{2WZ_0}$	$E_{CS} = X_{CS} \sqrt{\frac{2W}{Z_1}}$ <p style="text-align: center;">or</p> $E_{CS} = X_{CS} \sqrt{\frac{2W}{K^2 Z_2}}$ <p style="text-align: center;">whichever is larger</p>

TABLE II

Circuit-element inductance and capacitance for two-band networks for 3.5 and 7 Mc., 7 and 14 Mc., or 14 and 28 Mc., with an antenna having driving-point impedances of 75 and 1500 ohms at f_1 and f_2 respectively, using a 53-, 75- or 300-ohm transmission line.

Line Z_0	General Case	Schematic Diagram	Operating Frequencies											
			3.5 and 7 Mc.				7 and 14 Mc.				14 and 28 Mc.			
			L_P	L_S	C_P	C_S	L_P	L_S	C_P	C_S	L_P	L_S	C_P	C_S
53Ω (Example 1)	$Z_0 < Z_1 & Z_2$	Fig. 5	3.29 μh.	4.46 μh.	236 μfd.	396 μfd.	1.65 μh.	2.23 μh.	118 μfd.	198 μfd.	0.823 μh.	1.11 μh.	53.9 μfd.	98.9 μfd.
75Ω (Example 2)	$Z_0 = Z_1 < Z_2$	Fig. 6	31.2 μh.	4.86 μh.	66.2 μfd.	425 μfd.	15.6 μh.	2.43 μh.	33.1 μfd.	212 μfd.	7.82 μh.	1.22 μh.	16.5 μfd.	106 μfd.
300Ω (Example 3)	$Z_1 < Z_0 < Z_2$	Fig. 6	7.87 μh.	5.91 μh.	42.3 μfd.	233 μfd.	3.93 μh.	2.96 μh.	21.2 μfd.	118 μfd.	1.97 μh.	1.48 μh.	10.6 μfd.	58.5 μfd.

$$X_{LP} = 75 \sqrt{\frac{\left[(2^2)(1500) \right] - \left[\frac{75}{2^2} \right]}{\left[(2^2)(1500) \left(\frac{75}{75} - 1 \right) \right] + \left[75 \left(1 - \frac{75}{1500} \right) \right]}} = 687 \text{ ohms.}$$

$$X_{CP} = 2 \sqrt{\frac{\left[(2^2)(1500) \right] - \left[\frac{75}{2^2} \right]}{\left[(2^2)(75) \left(\frac{1500}{75} - 1 \right) \right] + \left[1500 \left(1 - \frac{75}{75} \right) \right]}} = 687 \text{ ohms.}$$

Since

$$X_{B1} = \frac{687}{1 + \left(\frac{687}{75} \right)^2} - \frac{687}{1 + \left(\frac{687}{75} \right)^2} = 0,$$

and

$$X_{B2} = \frac{(2)(687)}{(2^2) + \left(\frac{687}{1500} \right)^2} - \frac{(2)(687)}{1 + \left[\frac{(2)(687)}{75} \right]^2} = 322 \text{ ohms,}$$

$$X_{LS} = \frac{\left[(2)(322) \right] - [0]}{(2)(2^2 - 1)} = 107 \text{ ohms}$$

and

$$X_{CS} = 2 \frac{\left[322 \right] - \left[(2)(0) \right]}{(2)(2^2 - 1)} = 107 \text{ ohms.}$$

$$E_{CP} = \sqrt{(2)(1000)(1500)} = 1732 \text{ volts.}$$

$$\tan \phi = \frac{75}{687} = 0.109.$$

From trigonometry tables,

$$\phi = 6.25^\circ \text{ and } \cos \phi = 0.9941.$$

Then,

$$E_{CS} = 107 \frac{\sqrt{(2)(1000)(75)}}{(75)(0.9941)} = 556 \text{ volts.}$$

Example 3

Given: Same as *Example 1*, except that the line has a characteristic impedance of 300 ohms.

Solution: As in the other two examples, $K = 2$. With $Z_0 = 300$, $Z_1 = 75$ and $Z_2 = 1500$ ohms, this example falls into the general class of $Z_1 < Z_0 < Z_2$. Table I shows that the network of Fig. 6 and its associated formulas are suitable. Assigning numerical values to the formulas:

$$X_{LP} = 300 \sqrt{\frac{\left[(2^2)(1500) \right] - \left[\frac{75}{2^2} \right]}{\left[(2^2)(1500) \left(\frac{300}{75} - 1 \right) \right] + \left[75 \left(1 - \frac{300}{1500} \right) \right]}} = 173 \text{ ohms.}$$

$$X_{CP} = 2 \sqrt{\frac{\left[(2^2)(1500) \right] - \left[\frac{75}{2^2} \right]}{(75)(1500) \left[(2^2)(75) \left(\frac{1500}{300} - 1 \right) \right] + \left[(1500) \left(1 - \frac{75}{300} \right) \right]}} = 1075 \text{ ohms.}$$

TABLE III

*Coil Form — Number of Turns***

L μh.	Coil Form — Number of Turns**								
	A	B	C	D	E	F	G	H	I
0.823	5	3	6	10	6	6	3	3	3
1.11	7	3	7	12	8	7	3	3	4
1.22	7	3	8	13	9	7	4	3	4
1.48	8	4	9	14	9	8	4	4	4
1.65	8	5	9	15	10	9	5	4	5
1.97	9	5	10	16	11	9	5	4	5
2.23	9	5	10	17	11	10	6	5	6
2.43	10	5	11	18	12	11	6	5	6
2.96	11	6	12	20	13	12	7	6	7
3.29	12	7	12	20	14	12	8	6	8
3.93	12	8	14	23	15	13	8	7	8
4.46	13	7	15	24	16	14	9	8	9
4.86	14	9	15	25	17	15	9	8	9
5.91	15	10	17	27	19	16	11	10	11
7.82	18	12	19	32	21	19	13	12	14
7.87	18	12	19	32	21	19	13	12	14
15.6	25	21	27	44	30	26	22	18	22
31.2	35	*15	39	64	42	38	41	33	40

- A — 1½ inches diameter, 1½ inches long.
- B — 2½ inches diameter, 7 turns per inch (National XR10A form).
- C — 1¾ inches diameter, 2¾ inches long (National XR13 form).
- D — 1 inch diameter, 2¾ inches long (National XR13A form).
- E — 1½ inches diameter, 1¾ inches long (National XR16 form).
- F — 1¾ inches diameter, 3 inches long (Millen 44000 form).
- G — 2½ inches diameter, 6 turns per inch (B & W 3905).
- H — 2½ inches diameter, 8 turns per inch (B & W 3906).
- I — 2 inches diameter, 10 turns per inch (B & W 3907).
- * 5 inches diameter, 8 turns per inch (National XR14A form).
- ** To nearest turn.

Since

$$X_{B1} = \frac{1075}{1 + \left(\frac{1075}{75} \right)^2} - \frac{173}{1 + \left(\frac{173}{300} \right)^2} = -125 \text{ ohms}$$

and

$$X_{B2} = \frac{(2)(1075)}{2^2 + \left(\frac{1075}{1500} \right)^2} - \frac{(2)(173)}{1 + \left[\frac{(2)(173)}{300} \right]^2} = 328 \text{ ohms,}$$

$$X_{Ls} = \frac{[(2)(328)] - [-125]}{(2)(2^2 - 1)} = 130 \text{ ohms,}$$

and

$$X_{Cs} = 2 \frac{[328] - [(2)(-125)]}{(2)(2^2 - 1)} = 193 \text{ ohms.}$$

$$E_{CP} = \sqrt{(2)(1000)(1500)} = 1732 \text{ volts.}$$

$$\tan \phi = \frac{300}{173} = 1.73.$$

From trigonometry tables, $\phi = 60^\circ$ and $\cos \phi = 0.5$.

Then,

$$E_{CS} = 193 \frac{\sqrt{(2)(1000)(300)}}{(300)(0.5)} = 996 \text{ volts.}$$


The reactance values computed in these three examples are valid at the f_1 frequency of any pair of operating frequencies providing that $K = 2$. They could have been worked out for other values of K , of course. However, in such a case, Z_2 might be considerably different from 1500 ohms. Converting the values of reactance shown to inductance and capacitance at 3.5 Mc. permits two-band operation at 3.5 and 7 Mc. Converting them at 7 Mc. provides for operation at 7 and 14 Mc., etc.

Table II shows the values of inductance and capacitance (ordinary slide-rule accuracy) of the network elements in these three examples, for operation at 3.5 and 7 Mc., 7 and 14 Mc., and 14

(Continued on page 90)

CABINETS • CHASSIS • PANELS • RACKS

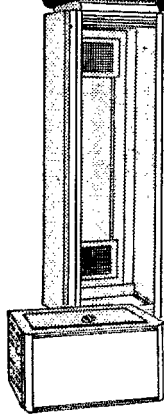BUILDING Electronic Equipment? SAVE MONEY and TIME with PAR-METAL HOUSINGS!
They're Standardized!



- **READY-TO-USE**
- **LOW IN COST**

There's a Par-Metal Housing for every purpose, from a small receiver to a deluxe transmitter.

You may order Par-Metal units practically from stock, thus eliminating the need for special made-to-order equipment on many jobs. Remember, Par-Metal equipment is made by electronic specialists, not just a sheet metal shop.


We offer an extensive selection of units for Manufacturers, Service Men, P.A. Men, Amateurs, etc.



PAR-METAL

PRODUCTS CORPORATION
32-52 — 49th ST., LONG ISLAND CITY 3, N. Y.
Export Dept., Rocke International Corp
13 East 40 Street, New York 16

WRITE FOR CATALOG

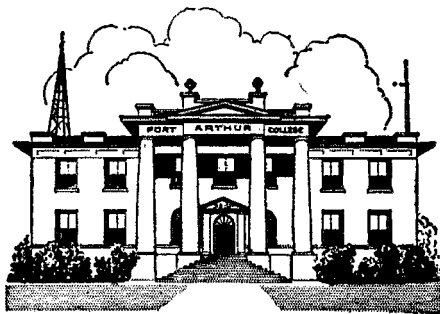

Founded in 1909

**RADIO TELEPHONY
RADIO TELEGRAPHY**

Courses ranging in length from 7 to 12 months. Dormitory room and board on campus for \$40.00 a month. The college owns KPAC, 5 KW broadcast station with studios located on campus. New students accepted monthly. If interested in radio training necessary to pass F.C.C. examinations for first-class telephone and second-class telegraph licenses, write for details.

PORT ARTHUR COLLEGE PORT ARTHUR TEXAS
Approved for G. I. training

Hints & Kinks

(Continued from page 33)

simply. The filament pins, which extend out of the base of the tube, are just the right size and spacing to fit snugly in a crystal socket designed for the new small crystal holders (1/2-inch spacing, 0.125-inch diameter pins). For grid and plate "caps" the pins can be removed from an Amphenol type 54 miniature socket and slipped over the pins of the tube. — Tom McMillen, W1QVF

Antenna-Matching Networks

(Continued from page 39)

and 28 Mc. D.p.i. values of 75 and 1500 ohms are assumed for f_1 and f_2 respectively. These values correspond closely to those of a simple center-fed antenna operating at its fundamental and second-harmonic frequencies. While actual practical values may depart somewhat, the values shown are likely to be close enough for all practical purposes, unless an extremely-low s.w.r. is demanded.

Table III shows several coil dimensions for each of the inductance values given in Table II. These dimensions were chosen to fit various standard coil forms or manufactured strip coils. They are given to the nearest full turn.

How's DX

(Continued from page 45)

fire is CN8ET, manned by W3KZQ. Walt used to be pre-war KB6RSJ, you know, and is enjoying the pleasures of a U. S.-oriented umpty-hundred-foot Vee array No sooner do we mention W4MR's 7-Mc. ground-plane than he takes it down again due to its adverse effect on the 20-meter beam. Al gives an account of N. C. DX activity in noting that W4GQU quit 20 c.w. for 10 'phone after confirming 101, W4AIT has a new AC4-working 3-element



Aurelio Flores of CX6AD is one of the more active Uruguayan fellows on 14-Mc. c.w. (Photo courtesy W9UOX)

beam, and W4GG keeps his 250-TL almost exclusively on 20 aided and abetted by a couple of stacked collinears VP5BF has swapped his 15-watt 807 Tri-tet oscillator for a 6V6-807 60-watter, according to W4LVV. Ken is contemplating giving the Caicos a good representation on 20, 40 and 80 this season after working all call areas but W7 with the QRP effort Adding a Guantanamo note, KG4AG keeps schedules with his dad, W9ZMK, of Rock Island, Ill. W9AND learns that VP1WS is rather

(Continued on page 98)